

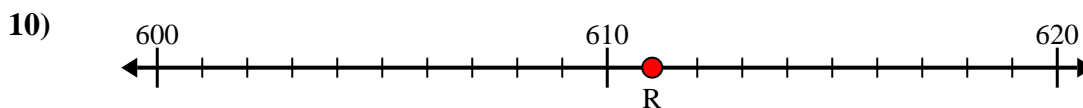
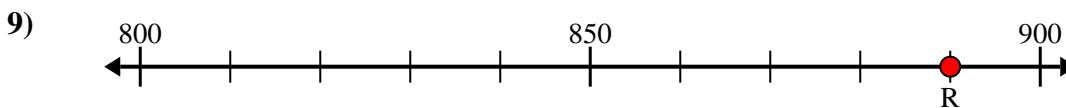
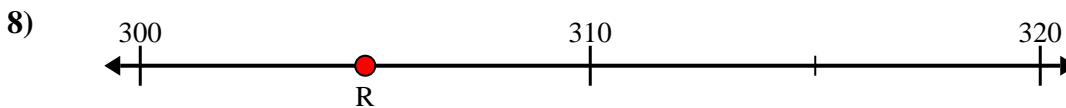
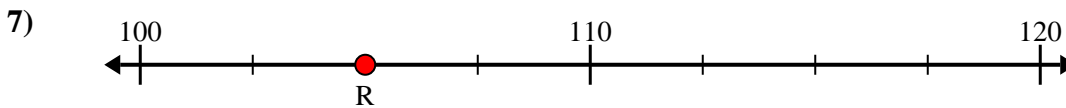
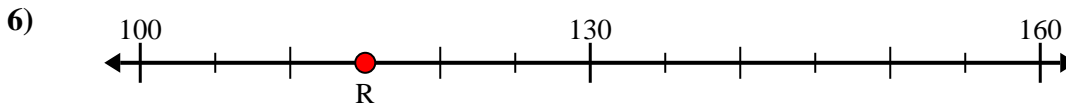
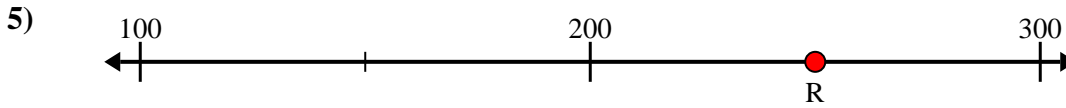
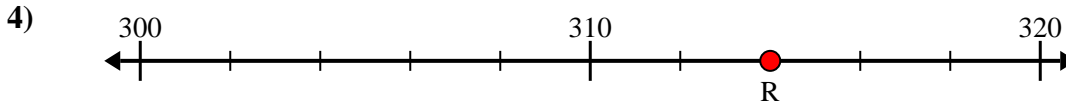
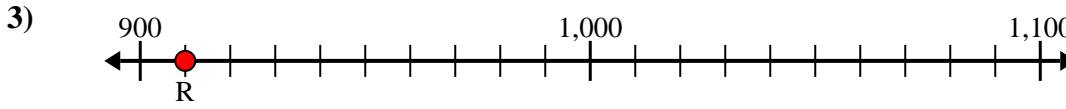


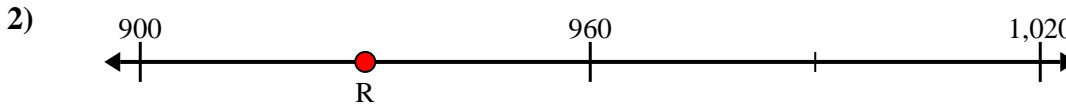

Find the value of R.










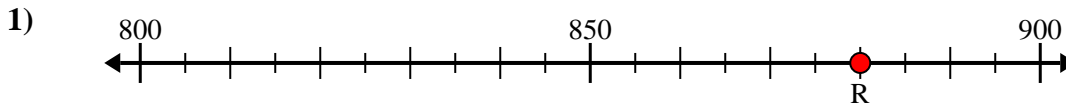


Answers

- 1. _____
- 2. _____
- 3. _____
- 4. _____
- 5. _____
- 6. _____
- 7. _____
- 8. _____
- 9. _____
- 10. _____



Find the value of R.

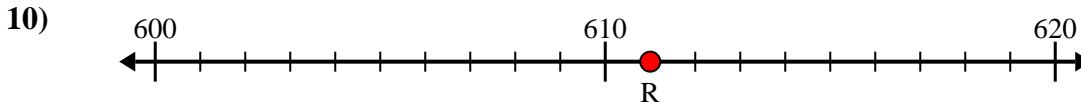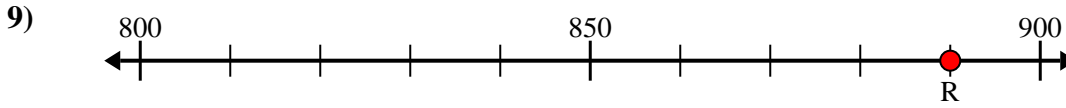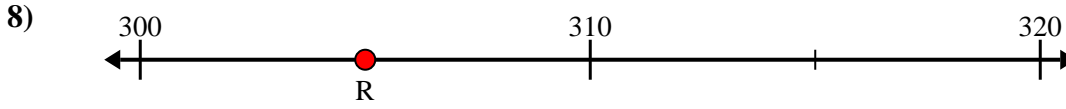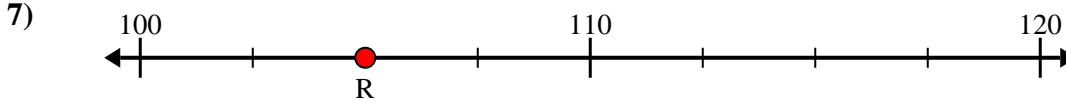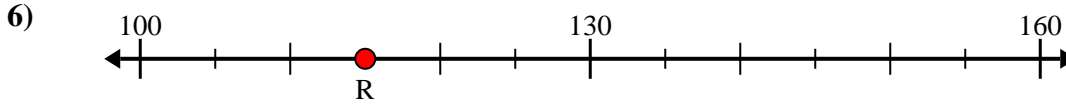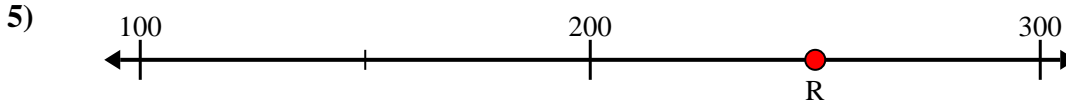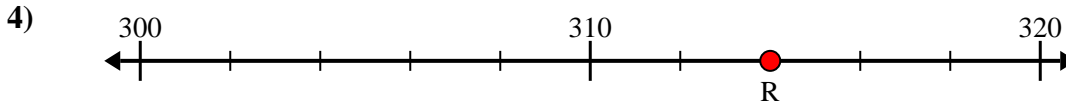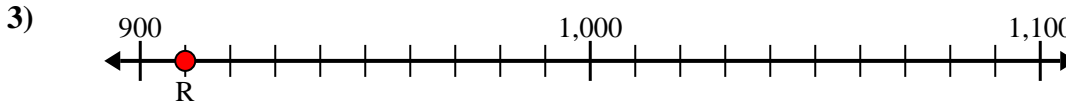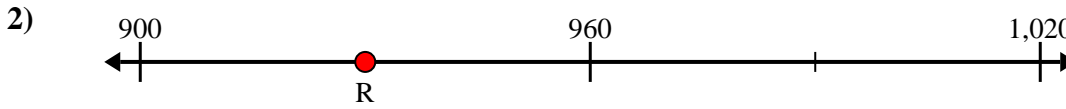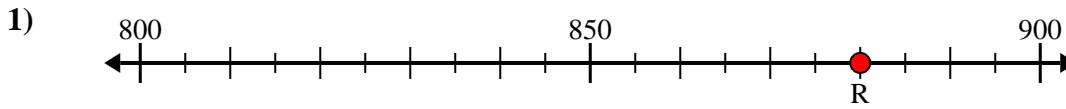

Answers

1. 880

2. 930

3. 910

4. 314

5. 250

6. 115

7. 105

8. 305

9. 890

10. 611